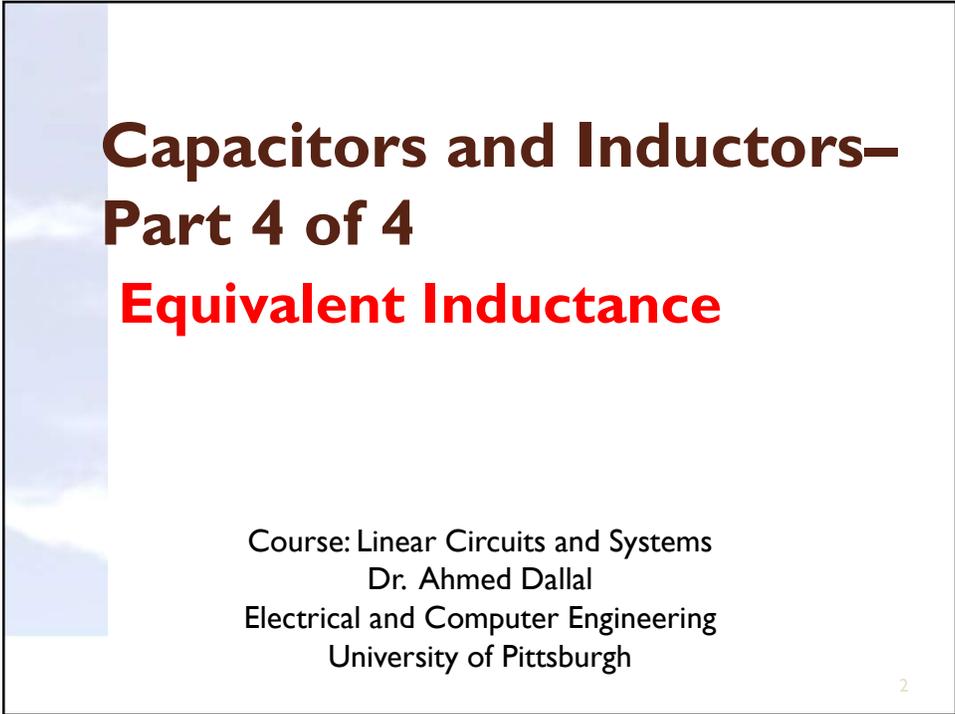


- Linear Circuits and Systems



## Capacitors and Inductors— Part 4 of 4

### Equivalent Inductance

Course: Linear Circuits and Systems  
Dr. Ahmed Dallal  
Electrical and Computer Engineering  
University of Pittsburgh

2


## Reminder: Voltage-current relationship

Inductor is a dynamic element whose voltage current relationship is given as:

$$v = L \frac{di}{dt} \qquad i = \frac{1}{L} \int v dt$$
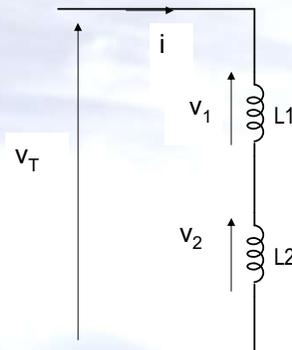
## Inductors in series

- What is the equivalent inductance of two inductors in series?



## Inductors in series


$$v = L \frac{di}{dt}$$

$$v_T = v_1 + v_2$$

$$L_T \frac{di}{dt} = L_1 \frac{di}{dt} + L_2 \frac{di}{dt}$$


$$L_T = L_1 + L_2$$

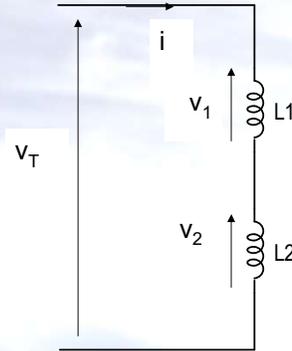In general  $L_T = L_1 + L_2 + \dots + L_n$


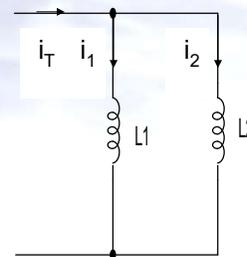
## Inductors in parallel

- What is the equivalent inductance of two inductors in parallel?



## Inductors in parallel

$$i = \frac{1}{L} \int v dt$$


$$i_T = i_1 + i_2$$

$$\frac{1}{L_T} \int v dt = \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2}$$

In general
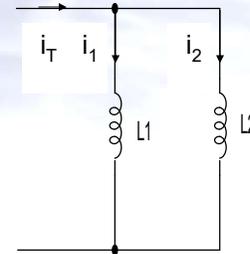
$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$




## Example

Effective inductance between A and B is:

$$L_s = L_2 + L_3 = 25 + 15 = 40 \text{ mH}$$

$$L_t = (L_1 \times L_s) / (L_1 + L_s)$$
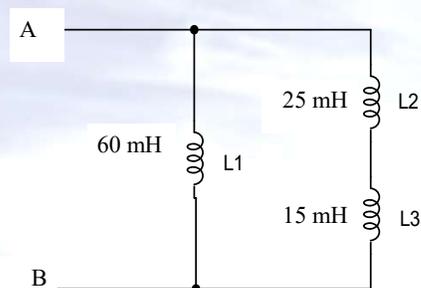
$$= (60 \times 40) / (60 + 40) = 24 \text{ mH}$$



## Conclusion



## Acknowledgement

This material is based upon work partially supported by the National Science Foundation under Grant# 2335802. Any opinions, findings, and conclusions, or recommendations expressed in this material are those of the author(s) and do not necessarily reflect the views of the National Science Foundation.



You are free

- to **Share** – to copy, distribute, display and perform the work
- to **Remix** – to make derivative works

Under the following conditions

- **Attribution** — You must attribute the work in the manner specified by the author or licensor (but not in any way that suggests that they endorse you or your use of the work).
- **Noncommercial** — You may not use this work for commercial purposes.
- **Share Alike** — If you alter, transform, or build upon this work, you may distribute the resulting work only under the same or similar license to this one.



**THE END**